

Chapter 4

- 4.1. SOP form: $f = \bar{x}_1x_2 + \bar{x}_2x_3$
 POS form: $f = (\bar{x}_1 + \bar{x}_2)(x_2 + x_3)$
- 4.2. SOP form: $f = x_1\bar{x}_2 + x_1x_3 + \bar{x}_2x_3$
 POS form: $f = (x_1 + x_3)(x_1 + \bar{x}_2)(\bar{x}_2 + x_3)$
- 4.3. SOP form: $f = \bar{x}_1x_2x_3\bar{x}_4 + x_1x_2\bar{x}_3x_4 + \bar{x}_2x_3x_4$
 POS form: $f = (\bar{x}_1 + x_4)(x_2 + x_3)(\bar{x}_2 + \bar{x}_3 + \bar{x}_4)(x_2 + x_4)(x_1 + x_3)$
- 4.4. SOP form: $f = \bar{x}_2\bar{x}_3 + \bar{x}_2\bar{x}_4 + x_2x_3x_4$
 POS form: $f = (\bar{x}_2 + x_3)(x_2 + \bar{x}_3 + \bar{x}_4)(\bar{x}_2 + x_4)$
- 4.5. SOP form: $f = \bar{x}_3\bar{x}_5 + \bar{x}_3x_4 + x_2x_4\bar{x}_5 + \bar{x}_1x_3\bar{x}_4x_5 + x_1x_2\bar{x}_4x_5$
 POS form: $f = (\bar{x}_3 + x_4 + x_5)(\bar{x}_3 + \bar{x}_4 + \bar{x}_5)(x_2 + \bar{x}_3 + \bar{x}_4)(x_1 + x_3 + x_4 + \bar{x}_5)(\bar{x}_1 + x_2 + x_4 + \bar{x}_5)$
- 4.6. SOP form: $f = \bar{x}_2x_3 + \bar{x}_1x_5 + \bar{x}_1x_3 + \bar{x}_3\bar{x}_4 + \bar{x}_2x_5$
 POS form: $f = (\bar{x}_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_4)(x_3 + \bar{x}_4 + x_5)$
- 4.7. SOP form: $f = x_3\bar{x}_4\bar{x}_5 + \bar{x}_3\bar{x}_4x_5 + x_1x_4x_5 + x_1x_2x_4 + x_3x_4x_5 + \bar{x}_2x_3x_4 + x_2\bar{x}_3x_4\bar{x}_5$
 POS form: $f = (x_3 + x_4 + x_5)(\bar{x}_3 + x_4 + \bar{x}_5)(x_1 + \bar{x}_2 + \bar{x}_3 + \bar{x}_4 + x_5)$
- 4.8. $f = \sum m(0, 7)$
 $f = \sum m(1, 6)$
 $f = \sum m(2, 5)$
 $f = \sum m(0, 1, 6)$
 $f = \sum m(0, 2, 5)$
 etc.
- 4.9. $f = x_1x_2x_3 + x_1x_2x_4 + x_1x_3x_4 + x_2x_3x_4$
- 4.10. SOP form: $f = x_1x_2\bar{x}_3 + x_1\bar{x}_2x_4 + x_1x_3\bar{x}_4 + \bar{x}_1x_2x_3 + \bar{x}_1x_3x_4 + x_2\bar{x}_3x_4$
 POS form: $f = (x_1 + x_2 + x_3)(x_1 + x_2 + x_4)(x_1 + x_3 + x_4)(x_2 + x_3 + x_4)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \bar{x}_4)$
 The POS form has lower cost.
- 4.11. The statement is false. As a counter example consider $f(x_1, x_2, x_3) = \sum m(0, 5, 7)$.
 Then, the minimum-cost SOP form $f = x_1x_3 + \bar{x}_1\bar{x}_2\bar{x}_3$ is unique.
 But, there are two minimum-cost POS forms:
 $f = (x_1 + \bar{x}_3)(\bar{x}_1 + x_3)(x_1 + \bar{x}_2)$ and
 $f = (x_1 + \bar{x}_3)(\bar{x}_1 + x_3)(\bar{x}_2 + x_3)$

4.12. If each circuit is implemented separately:

$$f = \overline{x_1}\overline{x_4} + \overline{x_1}x_2x_3 + x_1\overline{x_2}x_4 \quad \text{Cost} = 15$$

$$g = \overline{x_1}\overline{x_3}\overline{x_4} + \overline{x_2}x_3\overline{x_4} + x_1\overline{x_3}x_4 + x_1x_2x_4 \quad \text{Cost} = 21$$

In a combined circuit:

$$f = \overline{x_2}x_3\overline{x_4} + \overline{x_1}\overline{x_3}\overline{x_4} + x_1\overline{x_2}\overline{x_3}x_4 + \overline{x_1}x_2x_3$$

$$g = \overline{x_2}x_3\overline{x_4} + \overline{x_1}\overline{x_3}\overline{x_4} + x_1\overline{x_2}\overline{x_3}x_4 + x_1x_2x_4$$

The first 3 product terms are shared, hence the total cost is 31.

4.13. If each circuit is implemented separately:

$$f = \overline{x_1}x_2x_4 + x_2x_4x_5 + x_3\overline{x_4}\overline{x_5} + \overline{x_1}\overline{x_2}\overline{x_4}x_5 \quad \text{Cost} = 22$$

$$g = \overline{x_3}\overline{x_5} + \overline{x_4}\overline{x_5} + \overline{x_1}\overline{x_2}\overline{x_4} + \overline{x_1}x_2x_4 + x_2x_4x_5 \quad \text{Cost} = 24$$

In a combined circuit:

$$f = \overline{x_1}x_2x_4 + x_2x_4x_5 + x_3\overline{x_4}\overline{x_5} + \overline{x_1}\overline{x_2}\overline{x_4}x_5$$

$$g = \overline{x_1}x_2x_4 + x_2x_4x_5 + x_3\overline{x_4}\overline{x_5} + \overline{x_1}\overline{x_2}\overline{x_4}x_5 + \overline{x_3}\overline{x_5}$$

The first 4 product terms are shared, hence the total cost is 31. Note that in this implementation $f \subseteq g$, thus g can be realized as $g = f + \overline{x_3}\overline{x_5}$, in which case the total cost is lowered to 28.

4.14. $f = (x_3 \uparrow g) \uparrow ((g \uparrow g) \uparrow x_4)$ where $g = (x_1 \uparrow (x_2 \uparrow x_2)) \uparrow ((x_1 \uparrow x_1) \uparrow x_2)$

4.15. $\overline{f} = (((x_3 \downarrow x_3) \downarrow g) \downarrow ((g \downarrow g) \downarrow (x_4 \downarrow x_4)))$, where
 $g = ((x_1 \downarrow x_1) \downarrow x_2) \downarrow (x_1 \downarrow (x_2 \downarrow x_2))$. Then, $f = \overline{\overline{f}} \downarrow \overline{f}$.

4.16. $f = (g \uparrow k) \uparrow ((g \uparrow g) \uparrow (k \uparrow k))$, where $g = (x_1 \uparrow x_1) \uparrow (x_2 \uparrow x_2) \uparrow (x_5 \uparrow x_5)$
and $k = (x_3 \uparrow (x_4 \uparrow x_4)) \uparrow ((x_3 \uparrow x_3) \uparrow x_4)$

4.17. $\overline{f} = (g \downarrow k) \downarrow ((g \downarrow g) \downarrow (k \downarrow k))$, where $g = x_1 \downarrow x_2 \downarrow x_5$
and $k = ((x_3 \downarrow x_3) \downarrow x_4) \downarrow (x_3 \downarrow (x_4 \downarrow x_4))$. Then, $f = \overline{\overline{f}} \downarrow \overline{f}$.

4.18. $f = \overline{x_1}(x_2 + x_3)(x_4 + x_5) + x_1(\overline{x_2} + x_3)(\overline{x_4} + x_5)$

4.19. $f = x_1\overline{x_3}\overline{x_4} + x_2\overline{x_3}\overline{x_4} + x_1x_3x_4 + x_2x_3x_4 = (x_1 + x_2)\overline{x_3}\overline{x_4} + (x_1 + x_2)x_3x_4$
This requires 2 OR and 2 AND gates.

4.20. $f = x_1 \cdot g + \overline{x_1} \cdot \overline{g}$, where $g = \overline{x_3}x_4 + x_3\overline{x_4}$

4.21. $f = g \cdot h + \overline{g} \cdot \overline{h}$, where $g = x_1x_2$ and $h = x_3 + x_4$

4.22. Let $D(0, 20)$ be 0 and $D(15, 26)$ be 1. Then decomposition yields:

$$g = x_5(\overline{x_1} + x_2)$$

$$f = (\overline{x_3}\overline{x_4} + x_3x_4)g + \overline{x_3}x_4\overline{g} = x_3x_4g + \overline{x_3}\overline{x_4}g + \overline{x_3}x_4\overline{g}$$

$$\text{Cost} = 9 + 18 = 27$$

The optimal SOP form is:

$$f = \overline{x}_3 x_4 \overline{x}_5 + \overline{x}_1 x_3 x_4 x_5 + x_1 \overline{x}_2 \overline{x}_3 x_4 + \overline{x}_1 \overline{x}_3 \overline{x}_4 x_5 + x_2 \overline{x}_3 \overline{x}_4 x_5 + x_2 x_3 x_4 x_5$$

$$\text{Cost} = 7 + 29 = 36$$

4.23. The prime implicants are generated as follows:

List 1			List 2		
0	0 0 0 0	✓	0,2	0 0 x 0	
2	0 0 1 0	✓	0,4	0 x 0 0	
4	0 1 0 0	✓	0,8	x 0 0 0	
8	1 0 0 0	✓	4,5	0 1 0 x	
5	0 1 0 1	✓	8,9	1 0 0 x	
9	1 0 0 1	✓	5,7	0 1 x 1	
7	0 1 1 1	✓	7,15	x 1 1 1	
15	1 1 1 1	✓			

The initial prime implicant table is

Prime implicant	Minterm							
	0	2	4	5	7	8	9	15
$p_1 = 0 0 x 0$	✓	✓						
$p_2 = 0 x 0 0$	✓		✓					
$p_3 = x 0 0 0$	✓						✓	
$p_4 = 0 1 0 x$			✓	✓				
$p_5 = 1 0 0 x$							✓	✓
$p_6 = 0 1 x 1$				✓	✓			
$p_7 = x 1 1 1$					✓			✓

The prime implicants p_1 , p_5 and p_7 are essential. Removing these prime implicants gives

Prime implicant	Minterm	
	4	5
p_2	✓	
p_3		
p_4	✓	✓
p_6		✓

Since p_4 covers both minterms, the final cover is

$$\begin{aligned} C &= \{p_1, p_4, p_5, p_7\} \\ &= \{00x0, 010x, 100x, x111\} \end{aligned}$$

and the function is implemented as

$$f = \overline{x}_1\overline{x}_2\overline{x}_4 + \overline{x}_1x_2\overline{x}_3 + x_1\overline{x}_2\overline{x}_3 + x_2x_3x_4$$

4.24. The prime implicants are generated as follows:

List 1			List 2			List 3		
0	0 0 0 0	✓	0,4	0 x 0 0		3,7,11,15	x x 1 1	
4	0 1 0 0	✓	0,8	x 0 0 0		9,11,13,15	1 x x 1	
8	1 0 0 0	✓	4,6	0 1 x 0				
			8,9	1 0 0 x				
3	0 0 1 1	✓	3,7	0 x 1 1	✓			
6	0 1 1 0	✓	3,11	x 0 1 1	✓			
9	1 0 0 1	✓	6,7	0 1 1 x				
7	0 1 1 1	✓	9,11	1 0 x 1	✓			
11	1 0 1 1	✓	9,13	1 x 0 1	✓			
13	1 1 0 1	✓						
15	1 1 1 1	✓	7,15	x 1 1 1	✓			
			11,15	1 x 1 1	✓			
			13,15	1 1 x 1	✓			

The initial prime implicant table is

Prime implicant	Minterm					
	0	4	6	8	9	15
$p_1 = 0 x 0 0$	✓	✓				
$p_2 = x 0 0 0$	✓			✓		
$p_3 = 0 1 x 0$		✓	✓			
$p_4 = 1 0 0 x$				✓	✓	
$p_5 = 0 1 1 x$			✓			
$p_6 = x x 1 1$						✓
$p_7 = 1 x x 1$					✓	✓

There are no essential prime implicants. Prime implicant p_3 dominates p_5 and their costs are the same, so remove p_5 . Similarly, p_7 dominates p_6 , so remove p_6 . This gives

Prime implicant	Minterm					
	0	4	6	8	9	15
p_1	✓	✓				
p_2	✓			✓		
p_3		✓	✓			
p_4				✓	✓	
p_7					✓	✓

Now, p_3 and p_7 are essential, which leaves

Prime implicant	Minterm 0 8	
p_1	✓	
p_2	✓	✓
p_4		✓

Choosing p_2 results in the minimum cost cover

$$\begin{aligned} C &= \{p_2, p_3, p_7\} \\ &= \{x000, 01x0, 1xx1\} \end{aligned}$$

and the function is implemented as

$$f = \overline{x}_2\overline{x}_3\overline{x}_4 + \overline{x}_1x_2\overline{x}_4 + x_1x_4$$

4.25. The prime implicants are generated as follows:

List 1			List 2			List 3		
0	0 0 0 0	✓	0,4 0,8	0 x 0 0 x 0 0 0	✓	0,4,8,12	x x 0 0	
4	0 1 0 0	✓	4,5	0 1 0 x	✓	4,5,12,13	x 1 0 x	
8	1 0 0 0	✓	4,12	x 1 0 0	✓	8,9,12,13	1 x 0 x	
3	0 0 1 1	✓	8,9	1 0 0 x	✓			
5	0 1 0 1	✓	8,12	1 x 0 0	✓			
9	1 0 0 1	✓						
12	1 1 0 0	✓	3,7	0 x 1 1				
7	0 1 1 1	✓	3,11	x 0 1 1				
11	1 0 1 1	✓	5,7	0 1 x 1				
13	1 1 0 1	✓	5,13	x 1 0 1	✓			
14	1 1 1 0	✓	9,11	1 0 x 1				
			9,13	1 x 0 1	✓			
			12,13	1 1 0 x	✓			
			12,14	1 1 x 0				

The initial prime implicant table is

Prime implicant	Minterm					
	0	3	4	5	7	9 11
$p_1 = 0 \ x \ 1 \ 1$		✓			✓	
$p_2 = x \ 0 \ 1 \ 1$		✓				✓
$p_3 = 0 \ 1 \ x \ 1$				✓	✓	
$p_4 = 1 \ 0 \ x \ 1$						✓ ✓
$p_5 = x \ x \ 0 \ 0$	✓		✓			
$p_6 = x \ 1 \ 0 \ x$			✓	✓		
$p_7 = 1 \ x \ 0 \ x$						✓
$p_8 = 1 \ 1 \ x \ 0$						

Prime implicant p_5 is essential, so remove columns 0 and 4 to get

Prime implicant	Minterm				
	3	5	7	9	11
p_1	✓		✓		
p_2	✓				✓
p_3		✓	✓		
p_4				✓	✓
p_6		✓			
p_7				✓	

Here, p_3 dominates p_6 , and p_4 dominates p_7 ; but costs of p_3 and p_4 are greater than the costs of p_6 and p_7 , respectively. So, use branching. First choose p_3 to be in the final cover, which leads to

Prime implicant	Minterm		
	3	9	11
p_1	✓		
p_2	✓		✓
p_4		✓	✓
p_6			
p_7		✓	

Now, choose p_2 and p_7 (lower cost than p_4) to cover the remaining minterms. The resulting cover is

$$\begin{aligned}
 C &= \{p_2, p_3, p_5, p_7\} \\
 &= \{x011, 01x1, xx00, 1x0x\}
 \end{aligned}$$

Next, assume that p_3 is not included in the final cover, which leads to

Prime implicant	Minterm				
	3	5	7	9	11
p_1	✓		✓		
p_2	✓				✓
p_4				✓	✓
p_6		✓			
p_7				✓	

Then p_6 is essential. Also, column 3 dominates 7, hence remove 3 giving

Prime implicant	Minterm		
	7	9	11
p_1	✓		
p_2			✓
p_4		✓	✓
p_7		✓	

Choose p_1 and p_4 , which results in the cover

$$\begin{aligned} C &= \{p_1, p_4, p_5, p_6\} \\ &= \{0x11, 10x1, xx00, x10x\} \end{aligned}$$

Both covers have the same cost, so choosing the first cover the function can be implemented as

$$f = \overline{x}_2 x_3 x_4 + \overline{x}_1 x_2 x_4 + \overline{x}_3 \overline{x}_4 + x_1 \overline{x}_3$$

Observe that if we had not taken the cost of prime implicants (rows) into account and pursued the dominance of p_3 over p_6 and p_4 over p_7 , then we would have removed p_6 and p_7 giving the following table

Prime implicant	Minterm				
	3	5	7	9	11
p_1	✓		✓		
p_2	✓				✓
p_3		✓	✓		
p_4				✓	✓

Now p_3 and p_4 are essential. Also choose p_1 , so that

$$\begin{aligned} C &= \{p_1, p_3, p_4, p_5\} \\ &= \{0x11, 01x1, 10x1, xx00\} \end{aligned}$$

The cost of this cover is greater by one literal compared to both covers derived above.

4.26. Note that $X \# Y = X \cdot \overline{Y}$. Therefore,

$$\begin{aligned}(A \cdot B) \# C &= A \cdot B \cdot \overline{C} \\ (A \# C) \cdot (B \# C) &= A \cdot \overline{C} \cdot B \cdot \overline{C} \\ &= A \cdot B \cdot \overline{C}\end{aligned}$$

Similarly,

$$\begin{aligned}(A + B) \# C &= (A + B) \cdot \overline{C} \\ &= A \cdot \overline{C} + B \cdot \overline{C} \\ (A \# C) + (B \# C) &= A \cdot \overline{C} + B \cdot \overline{C}\end{aligned}$$

4.27. The initial cover is $C^0 = \{0000, 0011, 0100, 0101, 0111, 1000, 1001, 1111\}$.

Using the *-product get the prime implicants

$$P = \{00x0, 0x00, x000, 010x, 01x1, 100x, x111\}.$$

The minimum cover is $C_{minimum} = \{00x0, 010x, 100x, x111\}$, which corresponds to $f = \overline{x}_1\overline{x}_2\overline{x}_3 + \overline{x}_1x_2\overline{x}_3 + x_1\overline{x}_2\overline{x}_3 + x_2x_3x_4$.

4.28. The initial cover is $C^0 = \{0x0x0, 110xx, x1101, 1001x, 11110, 01x10, 0x011\}$.

Using the *-product get the prime implicants

$$P = \{0x0x0, xx01x, x1x10, 110xx, x10x0, 11x01, x1101\}.$$

The minimum cover is $C_{minimum} = \{0x0x0, xx01x, x1x10, 110xx, x1101\}$, which corresponds to $f = \overline{x}_1\overline{x}_3\overline{x}_5 + \overline{x}_3x_4 + x_2x_4\overline{x}_5 + x_1x_2\overline{x}_3 + x_2x_3\overline{x}_4x_5$.

4.29. The initial cover is $C^0 = \{00x0, 100x, x010, 1111, 00x1, 011x\}$.

Using the *-product get the prime implicants $P = \{00xx, 0x1x, x00x, x0x0, x111\}$.

The minimum-cost cover is $C_{minimum} = \{x00x, x0x0, x111\}$, which corresponds to $f = \overline{x}_2\overline{x}_3 + \overline{x}_2\overline{x}_4 + x_2x_3x_4$.

4.30. Expansion of $\overline{x}_1\overline{x}_2\overline{x}_3$ gives \overline{x}_1 .

Expansion of $\overline{x}_1\overline{x}_2x_3$ gives \overline{x}_1 .

Expansion of $\overline{x}_1x_2\overline{x}_3$ gives \overline{x}_1 .

Expansion of $x_1x_2x_3$ gives x_2x_3 .

The set of prime implicants comprises \overline{x}_1 and x_2x_3 .

4.31. Expansion of $\overline{x}_1x_2\overline{x}_3x_4$ gives $x_2\overline{x}_3x_4$ and $\overline{x}_1x_2x_4$.

Expansion of $x_1x_2\overline{x}_3x_4$ gives $x_2\overline{x}_3x_4$.

Expansion of $x_1x_2x_3\overline{x}_4$ gives $x_3\overline{x}_4$.

Expansion of $\overline{x}_1x_2x_3$ gives \overline{x}_1x_3 .

Expansion of \overline{x}_2x_3 gives \overline{x}_2x_3 .

The set of prime implicants comprises $x_2\overline{x}_3x_4$, $\overline{x}_1x_2x_4$, $x_3\overline{x}_4$, \overline{x}_1x_3 , and \overline{x}_2x_3 .

4.32. Representing both functions in the form of Karnaugh map, it is easy to show that $f = g$. The minimum cost SOP expression is

$$f = g = \overline{x}_2\overline{x}_3\overline{x}_5 + \overline{x}_2x_3\overline{x}_4 + x_1x_3x_4 + x_1x_2x_4x_5.$$

- 4.33. The cost of the circuit in Figure P4.2 is 11 gates and 30 inputs, for a total of 41. The functions implemented by the circuit can also be realized as

$$\begin{aligned} f &= \overline{x_1}\overline{x_2}\overline{x_4} + x_2\overline{x_3}\overline{x_4} + \overline{x_1}x_3x_4 + x_1x_4 \\ g &= \overline{x_1}\overline{x_2}\overline{x_4} + x_2\overline{x_3}\overline{x_4} + \overline{x_1}x_3x_4 + \overline{x_2}x_4 + x_3\overline{x_4} \end{aligned}$$

The first three product terms in f and g are the same; therefore, they can be shared. Then, the cost of implementing f and g is 8 gates and 24 inputs, for a total of 32.

- 4.34. The cost of the circuit in Figure P4.3 is 11 gates and 26 inputs, for a total of 37. The functions implemented by the circuit can also be realized as

$$\begin{aligned} f &= (\overline{x_2} \uparrow x_4) \uparrow (\overline{x_1} \uparrow x_2 \uparrow x_3) \uparrow (x_1 \uparrow \overline{x_2} \uparrow x_3) \uparrow (\overline{x_2} \uparrow \overline{x_3}) \\ g &= (\overline{x_2} \uparrow x_4) \uparrow (\overline{x_1} \uparrow x_2 \uparrow x_3) \uparrow (x_1 \uparrow \overline{x_2} \uparrow x_3) \uparrow (\overline{x_1} \uparrow \overline{x_1}) \end{aligned}$$

The first three NAND terms in f and g are the same; therefore, they can be shared. Then, the cost of implementing f and g is 7 gates and 20 inputs, for a total of 27.

- 4.35. Using gate level primitives, the circuit in Figure 4.25b can be implemented using the code

```
module prob4_35 (x1, x2, x3, x4, x5, f);
  input x1, x2, x3, x4, x5;
  output f;

  or (g, x1, x2, x5);
  not (notx3, x3);
  not (notx4, x4);
  and (a, x3, notx4);
  and (b, notx3, x4);
  or (k, a, b);
  and (c, g, k);
  not (notg, g);
  not (notk, k);
  and (d, notg, notk);
  or (f, c, d);

endmodule
```

4.36. Using continuous assignment, the circuit in Figure 4.25*b* can be implemented using the code

```
module prob4_36 (x1, x2, x3, x4, x5, f);  
  input  x1, x2, x3, x4, x5;  
  output f;  
  wire g, k;  
  
  assign g = (x1 | x2 | x5);  
  assign k = (x3 & ~x4) | (~x3 & x4);  
  assign f = (g & k) | (~g & ~k);  
  
endmodule
```

4.37. Using gate level primitives, the circuit in Figure 4.27*c* can be implemented using the code

```
module prob4_37 (x1, x2, x3, x4, x5, x6, x7, f);  
  input  x1, x2, x3, x4, x5, x6, x7;  
  output f;  
  
  nand (a, x1, x1);  
  nand (b, x2, x3);  
  nand (c, a, b);  
  nand (d, x5, x5);  
  nand (e, x6, x6);  
  nand (g, d, e);  
  nand (h, x4, g);  
  nand (j, x7, x7);  
  nand (k, h, j);  
  nand (m, c, k);  
  nand (f, m, m);  
  
endmodule
```

4.38. Using continuous assignment, the circuit in Figure 4.27*c* can be implemented using the code

```
module prob4_38 (x1, x2, x3, x4, x5, x6, x7, f);  
  input  x1, x2, x3, x4, x5, x6, x7;  
  output f;  
  wire a, b;  
  
  assign a = ~(~x1 & ~(x2 & x3));  
  assign b = ~(~(x4 & ~(~x5 & ~x6)) & ~x7);  
  assign f = ~(~(a & b));  
  
endmodule
```

4.39. Using gate level primitives, the circuit in Figure 4.28*b* can be implemented using the code

```
module prob4_39 (x1, x2, x3, x4, x5, x6, x7, f);  
  input  x1, x2, x3, x4, x5, x6, x7;  
  output f;  
  
  nor (a, x2, x2);  
  nor (b, x3, x3);  
  nor (c, a, b);  
  nor (d, x1, c);  
  nor (e, x4, x4);  
  nor (g, x5, x6);  
  nor (h, e, g);  
  nor (k, h, x7);  
  nor (f, d, k);  
  
endmodule
```

4.40. Using continuous assignment, the circuit in Figure 4.27*c* can be implemented using the code

```
module prob4_40 (x1, x2, x3, x4, x5, x6, x7, f);  
  input  x1, x2, x3, x4, x5, x6, x7;  
  output f;  
  wire a, b;  
  
  assign a = ~(x1 | ~(~x2 | ~x3));  
  assign b = ~(~(~x4 | ~(x5 | x6)) | x7);  
  assign f = ~(a | b);  
  
endmodule
```

4.41. Using the POS expression

$$f = (x_1 + x_2 + \overline{x}_3 + \overline{x}_4)(x_1 + \overline{x}_2 + \overline{x}_3 + x_4)(\overline{x}_1 + x_2 + \overline{x}_3 + x_4)(\overline{x}_1 + \overline{x}_2 + x_3 + \overline{x}_4)$$

the function can be implemented using the code

```

module prob4_41 (x1, x2, x3, x4, f);
  input x1, x2, x3, x4;
  output f;

  not (notx1, x1);
  not (notx2, x2);
  not (notx3, x3);
  not (notx4, x4);
  or (a, x1, x2, notx3, notx4);
  or (b, x1, notx2, notx3, x4);
  or (c, notx1, x2, notx3, x4);
  or (d, notx1, notx2, x3, notx4);
  and (f, a, b, c, d);

endmodule

```

4.42. Using the POS expression

$$f = (x_1 + x_2 + \bar{x}_3 + \bar{x}_4)(x_1 + \bar{x}_2 + \bar{x}_3 + x_4)(\bar{x}_1 + x_2 + \bar{x}_3 + x_4)(\bar{x}_1 + \bar{x}_2 + x_3 + \bar{x}_4)$$

the function can be implemented using the code

```

module prob4_42 (x1, x2, x3, x4, f);
  input x1, x2, x3, x4;
  output f;

  assign f = (x1 | x2 | ~x3 | ~x4) & (x1 | ~x2 | ~x3 | x4) &
    (~x1 | x2 | ~x3 | x4) & (~x1 | ~x2 | x3 | ~x4);

endmodule

```

4.43. The simplest expression is

$$f = \bar{x}_1\bar{x}_3 + x_2x_3(x_1 + x_4)$$

which can be implemented using the code

```

module prob4_43 (x1, x2, x3, x4, f);
  input x1, x2, x3, x4;
  output f;

  not (notx1, x1);
  not (notx3, x3);
  and (a, notx1, notx3);
  or (b, x1, x4);
  and (c, x2, x3, b);
  or (f, a, c);

endmodule

```

4.44. The simplest expression is

$$f = \overline{x_1}\overline{x_3} + x_2x_3(x_1 + x_4)$$

which can be implemented using the code

```
module prob4_44 (x1, x2, x3, x4, f);  
  input  x1, x2, x3, x4;  
  output f;  
  
  assign f = (~x1 & ~x3) | (x2 & x3 & (x1 | x4));  
endmodule
```

4.45. The simplest expression is

$$f = (\overline{x_1} + x_3)(x_1 + \overline{x_2} + \overline{x_3} + x_4)$$

which can be implemented using the code

```
module prob4_45 (x1, x2, x3, x4, f);  
  input  x1, x2, x3, x4;  
  output f;  
  
  not (notx1, x1);  
  not (notx2, x2);  
  not (notx3, x3);  
  or (a, notx1, x3);  
  or (b, x1, notx2, notx3, x4);  
  and (f, a, b);  
  
endmodule
```

4.46. The simplest expression is

$$f = (\overline{x_1} + x_3)(x_1 + \overline{x_2} + \overline{x_3} + x_4)$$

which can be implemented using the code

```
module prob4_46 (x1, x2, x3, x4, f);  
  input  x1, x2, x3, x4;  
  output f;  
  
  assign f = (~x1 | x3) & (x1 | ~x2 | ~x3 | x4);  
  
endmodule
```

4.47. The simplest expression is

$$f = (x_2 + \overline{x}_3)(\overline{x}_1 + \overline{x}_3 + x_4)$$

which can be implemented using the code

```
module prob4_47 (x1, x2, x3, x4, f);  
  input  x1, x2, x3, x4;  
  output f;  
  
  not (notx1, x1);  
  not (notx3, x3);  
  or (a, x2, notx3);  
  or (b, notx1, notx3, x4);  
  and (f, a, b);  
  
endmodule
```

4.48. The simplest expression is

$$f = (x_2 + \overline{x}_3)(\overline{x}_1 + \overline{x}_3 + x_4)$$

which can be implemented using the code

```
module prob4_47 (x1, x2, x3, x4, f);  
  input  x1, x2, x3, x4;  
  output f;  
  
  assign f = (x2 | ~x3) & (~x1 | ~x3 | x4);  
endmodule
```