

# Chapter 8

8.1. The expressions for the inputs of the flip-flops are

$$\begin{aligned} D_2 &= Y_2 = \overline{w}y_2 + \overline{y}_1\overline{y}_2 \\ D_1 &= Y_1 = w \oplus y_1 \oplus y_2 \end{aligned}$$

The output equation is

$$z = y_1y_2$$

8.2. The excitation table for JK flip-flops is

Present state $y_2y_1$	Flip-flop inputs				Output $z$
	$w = 0$		$w = 1$		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	1d	0d	1d	1d	0
01	0d	d0	0d	d1	0
10	d0	1d	d1	0d	0
11	d0	d1	d1	d0	1

The expressions for the inputs of the flip-flops are

$$\begin{aligned} J_2 &= \overline{y}_1 \\ K_2 &= w \\ J_1 &= \overline{w}y_2 + w\overline{y}_2 \\ K_1 &= J_1 \end{aligned}$$

The output equation is

$$z = y_1y_2$$

8.3. A possible state table is

Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	E	C	0	0
C	E	D	0	0
D	E	D	0	1
E	F	B	0	0
F	A	B	0	1

8.4. Verilog code for the solution given in problem 8.3 is

```
module prob8_4 (Clock, Resetn, w, z);
  input Clock, Resetn, w;
  output z;
  reg z;
  reg [3:1] y, Y;
  parameter [3:1] A = 3'b000, B = 3'b001, C = 3'b010, D = 3'b011, E = 3'b100, F = 3'b101;
  // Define the next state and output combinational circuits
  always @(w or y)
    case (y)
      A: if (w) begin
          Y = B; z = 0;
        end
      else begin
          Y = A; z = 0;
        end
      B: if (w) begin
          Y = C; z = 0;
        end
      else begin
          Y = E; z = 0;
        end
      C: if (w) begin
          Y = D; z = 0;
        end
      else begin
          Y = E; z = 0;
        end
      D: if (w) begin
          Y = D; z = 1;
        end
      else begin
          Y = E; z = 0;
        end
      E: if (w) begin
          Y = B; z = 0;
        end
      else begin
          Y = F; z = 0;
        end
      F: if (w) begin
          Y = B; z = 1;
        end
      else begin
          Y = A; z = 0;
        end
      default: begin
          Y = 3'bxxx; z = 0;
        end
    endcase
```

```
// Define the sequential block
always @(negedge Resetn or posedge Clock)
    if (Resetn == 0) y <= A;
    else y <= Y;

endmodule
```

8.5. A minimal state table is

Present state	Next State		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	E	C	0
C	D	C	0
D	A	F	1
E	A	F	0
F	E	C	1

8.6. An initial attempt at deriving a state table may be

Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	D	C	0	0
C	D	C	1	0
D	A	E	0	1
E	D	C	0	0

States  $B$  and  $E$  are equivalent; hence the minimal state table is

Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	D	C	0	0
C	D	C	1	0
D	A	B	0	1

8.7. For Figure 8.51 have (using the straightforward state assignment):

	Present state $y_3y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_3Y_2Y_1$	$Y_3Y_2Y_1$	
A	0 0 0	0 0 1	0 1 0	1
B	0 0 1	0 1 1	1 0 1	1
C	0 1 0	1 0 1	1 0 0	0
D	0 1 1	0 0 1	1 1 0	1
E	1 0 0	1 0 1	0 1 0	0
F	1 0 1	1 0 0	0 1 1	0
G	1 1 0	1 0 1	1 1 0	0

This leads to

$$\begin{aligned}
 Y_3 &= \overline{w}y_3 + \overline{y}_1y_2 + wy_1\overline{y}_3 \\
 Y_2 &= wy_3 + w\overline{y}_1\overline{y}_2 + wy_1y_2 + \overline{w}y_1\overline{y}_2\overline{y}_3 \\
 Y_1 &= \overline{y}_3\overline{w} + \overline{y}_1\overline{w} + wy_1\overline{y}_2 \\
 z &= y_1\overline{y}_3 + \overline{y}_2\overline{y}_3
 \end{aligned}$$

For Figure 8.52 have

	Present state $y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2Y_1$	$Y_2Y_1$	
A	0 0	0 1	1 0	1
B	0 1	0 0	1 1	1
C	1 0	1 1	1 0	0
F	1 1	1 0	0 0	0

This leads to

$$\begin{aligned}
 Y_2 &= \overline{w}y_2 + \overline{y}_1y_2 + w\overline{y}_2 \\
 Y_1 &= \overline{y}_1\overline{w} + wy_1\overline{y}_2 \\
 z &= \overline{y}_2
 \end{aligned}$$

Clearly, minimizing the number of states leads to a much simpler circuit.

8.8. For Figure 8.55 have (using straightforward state assignment):

	Present state $y_4y_3y_2y_1$	Next state				Output $z$
		DN=00	01	10	11	
		$Y_4Y_3Y_2Y_1$				
S1	0 0 0 0	0 0 0 0	0 0 1 0	0 0 0 1	—	0
S2	0 0 0 1	0 0 0 1	0 0 1 1	0 1 0 0	—	0
S3	0 0 1 0	0 0 1 0	0 1 0 1	0 1 1 0	—	0
S4	0 0 1 1	0 0 0 0	—	—	—	1
S5	0 1 0 0	0 0 1 0	—	—	—	1
S6	0 1 0 1	0 1 0 1	0 1 1 1	1 0 0 0	—	0
S7	0 1 1 0	0 0 0 0	—	—	—	1
S8	0 1 1 1	0 0 0 0	—	—	—	1
S9	1 0 0 0	0 0 1 0	—	—	—	1

The next-state and output expressions are

$$\begin{aligned}
 Y_4 &= Dy_3 \\
 Y_3 &= Dy_1 + Dy_2 + Ny_2 + \overline{D}y_3\overline{y}_2y_1 \\
 Y_2 &= N\overline{y}_2 + y_3\overline{y}_1 + \overline{N}\overline{y}_3y_2\overline{y}_1 \\
 Y_1 &= Ny_2 + D\overline{y}_2\overline{y}_1 + \overline{D}\overline{y}_2y_1 \\
 z &= y_4 + y_1y_2 + \overline{y}_1y_3
 \end{aligned}$$

Using the same approach for Figure 8.56 gives

	Present state $y_3y_2y_1$	Next state				Output $z$
		DN=00	01	10	11	
		$Y_3Y_2Y_1$				
S1	0 0 0	0 0 0	0 1 0	0 0 1	—	0
S2	0 0 1	0 0 1	0 1 1	1 0 0	—	0
S3	0 1 0	0 1 0	0 0 1	0 1 1	—	0
S4	0 1 1	0 0 0	—	—	—	1
S5	1 0 0	0 1 0	—	—	—	1

The next-state and output expressions are:

$$\begin{aligned}
 Y_3 &= D\overline{y}_2y_1 \\
 Y_2 &= y_3 + \overline{N}y_2\overline{y}_1 + N\overline{y}_2 \\
 Y_1 &= \overline{D}\overline{y}_2y_1 + Ny_2\overline{y}_1 + D\overline{y}_3\overline{y}_1 \\
 z &= y_3 + y_2y_1
 \end{aligned}$$

These expressions define a circuit that has considerably lower cost than the circuit resulting from Figure 8.55.

8.9. To compare individual bits, let  $k = w_1 \oplus w_2$ . Then, a suitable state table is

Present state	Next state		Output $z$	
	$k = 0$	$k = 1$	$k = 0$	$k = 1$
A	B	A	0	0
B	C	A	0	0
C	D	A	0	0
D	D	A	1	0

The state-assigned table is

Present state $y_2y_1$	Next State		Output	
	$k = 0$	$k = 1$	$k = 0$	$k = 1$
	$Y_2Y_1$	$Y_2Y_1$	$z$	$z$
00	01	00	0	0
01	10	00	0	0
10	11	00	0	0
11	11	00	1	0

The next-state and output expressions are

$$\begin{aligned}
 Y_2 &= \bar{k}y_1 + \bar{k}y_2 \\
 Y_1 &= \bar{k}\bar{y}_1 + \bar{k}y_2 \\
 z &= \bar{k}y_1y_2
 \end{aligned}$$

8.10. Verilog code for the solution given in problem 8.9 is

```
module prob8_10 (Clock, Resetn, w1, w2, z);
  input Clock, Resetn, w1, w2;
  output z;
  reg z;
  reg [2:1] y, Y;
  wire k;
  parameter [2:1] A = 2'b00, B = 2'b01, C = 2'b10, D = 2'b11;

  // Define the next state and output combinational circuits
  assign k = w1 ^ w2;
  always @(k or y)
    case (y)
      A: if (k) begin
          Y = A; z = 0;
        end
        else begin
          Y = B; z = 0;
        end
      B: if (k) begin
          Y = A; z = 0;
        end
        else begin
          Y = C; z = 0;
        end
      C: if (k) begin
          Y = A; z = 0;
        end
        else begin
          Y = D; z = 0;
        end
      D: if (k) begin
          Y = A; z = 0;
        end
        else begin
          Y = D; z = 1;
        end
    endcase

  // Define the sequential block
  always @(negedge Resetn or posedge Clock)
    if (Resetn == 0) y <= A;
    else y <= Y;

endmodule
```

8.11. A possible minimum state table for a Moore-type FSM is

Present state	Next state		Output z
	w = 0	w = 1	
A	B	C	0
B	D	E	0
C	E	D	0
D	F	G	0
E	F	F	0
F	A	A	0
G	A	A	1

8.12. A minimum state table is shown below. We assume that the 3-bit patterns do not overlap.

Present state	Next state		Output p
	w = 0	w = 1	
A	B	C	0
B	D	E	0
C	E	D	0
D	A	F	0
E	F	A	0
F	B	C	1



8.13. Verilog code for the solution given in problem 8.12 is

```

module prob8_13 (Clock, Resetn, w, p);
  input Clock, Resetn, w;
  output p;
  reg [3:1] y, Y;
  parameter [3:1] A = 3'b000, B = 3'b001, C = 3'b010, D = 3'b011, E = 3'b100, F = 3'b101;


  // Define the next state combinational circuit
  always @(w or y)
    case (y)
      A: if (w) Y = C;
         else Y = B;
      B: if (w) Y = E;
         else Y = D;
      C: if (w) Y = D;
         else Y = E;
      D: if (w) Y = F;
         else Y = A;
      E: if (w) Y = A;
         else Y = F;
      F: if (w) Y = C;
         else Y = B;
      default: Y = 3'bxxx;
    endcase

  // Define the sequential block
  always @(negedge Resetn or posedge Clock)
    if (Resetn == 0) y <= A;
    else y <= Y;

  // Define output
  assign p = (y == F);
endmodule

```

8.14. The timing diagram is

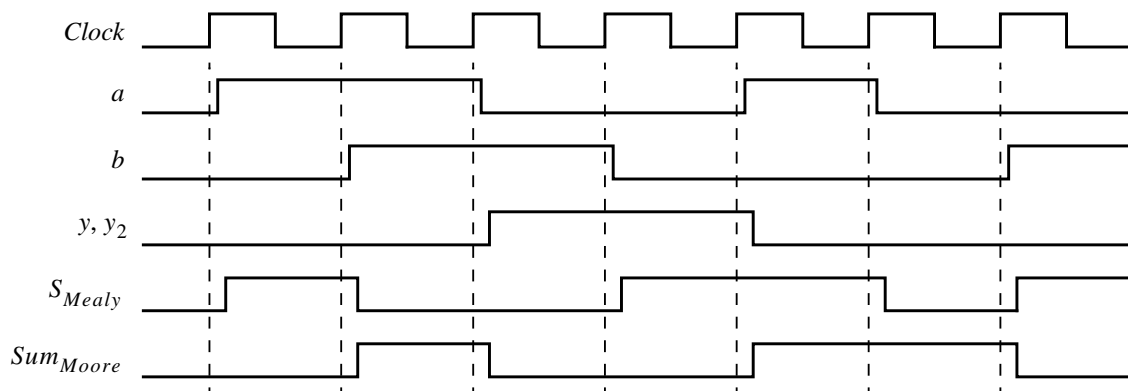

8.15. The state table corresponding to Figure P8.1 is

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	C	D	0
B	B	A	0
C	D	A	0
D	C	B	1

Using one-hot encoding, the state-assigned table is

	Present state	Next state		Output $z$
		$w = 0$	$w = 1$	
	$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$	$Y_4Y_3Y_2Y_1$	$z$
A	0 0 0 1	0 1 0 0	1 0 0 0	0
B	0 0 1 0	0 0 1 0	0 0 0 1	0
C	0 1 0 0	1 0 0 0	0 0 0 1	0
D	1 0 0 0	0 1 0 0	0 0 1 0	1

The next-state expressions are

$$\begin{aligned}
 D_4 &= Y_4 = \bar{w}y_3 + wy_1 \\
 D_3 &= Y_3 = \bar{w}(y_1 + y_4) \\
 D_2 &= Y_2 = \bar{w}y_2 + wy_4 \\
 D_1 &= Y_1 = w(y_2 + y_1)
 \end{aligned}$$

The output is given by  $z = y_4$ .

8.16. The state-assignment given in problem 8.15 can be used, except that the state variable  $y_1$  should be complemented. Thus, the state assignment will be  $y_4y_3y_2y_1 = 0000, 0011, 0101$ , and  $1001$ , for the states  $A, B, C$ , and  $D$ , respectively. The circuit derived in problem 8.15 can be used, except that the signal for the state variable  $y_1$  should be taken from the  $\bar{Q}$  output of flip-flop 1, rather than from its  $Q$  output.

8.17. The partitioning process gives

$$\begin{aligned}
 P_1 &= (ABCDEFGG) \\
 P_2 &= (ABD)(CEFG) \\
 P_3 &= (ABD)(CEG)(F) \\
 P_4 &= (ABD)(CEG)(F)
 \end{aligned}$$

The minimum state table is

Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	C	0	0
C	F	C	0	1
F	C	A	0	1

8.18. The partitioning process gives

$$P_1 = (ABCDEFGG)$$

$$P_2 = (ADG)(BCEF)$$

$$P_3 = (AG)(D)(B)(CE)(F)$$

$$P_4 = (A)(G)(D)(B)(CE)(F)$$

The minimized state table is

Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	B	C	0	0
B	D	—	0	1
C	F	C	0	1
D	B	G	0	0
F	C	D	0	1
G	F	—	0	0

8.19. An implementation for the Moore-type FSM in Figures 8.5.7 and 8.5.6 is given in the solution for problem 8.8. The Mealy-type FSM in Figure 8.5.8 is described in the form of a state table as

Present state	Next state				Output $z$			
	DN=00	01	10	11	00	01	10	11
S1	S1	S3	S2	—	0	0	0	1
S2	S2	S1	S3	—	0	1	1	—
S3	S3	S2	S1	—	0	0	1	—

The state-assigned table is

Present state $y_2y_1$	Next state				Output			
	DN=00	01	10	11	00	01	10	11
	$Y_2Y_1$	$Y_2Y_1$	$Y_2Y_1$	$Y_2Y_1$	$z$	$z$	$z$	$z$
00	00	10	01	—	0	0	0	—
01	01	00	10	—	0	1	1	—
10	10	01	00	—	0	0	1	—

The next-state and output expressions are

$$Y_2 = Dy_1 + \overline{D}y_2\overline{N} + N\overline{y}_2\overline{y}_1$$

$$Y_1 = Ny_2 + \overline{D}y_1\overline{N} + D\overline{y}_2\overline{y}_1$$

$$z = Dy_1 + Dy_2 + Ny_1$$

In this case, choosing the Mealy model results in a simpler circuit.

8.20. Use  $w$  as the clock. Then the state table is

Present state	Next state	Output $z_1z_0$
A	B	0 0
B	C	1 0
C	D	0 1
D	A	1 1

The state-assigned table is


Present state $y_1y_0$	Next state $Y_1Y_0$	Output $z_1z_0$
0 0	1 0	0 0
1 0	0 1	1 0
0 1	1 1	0 1
1 1	0 0	1 1

The next-state expressions are

$$Y_1 = \overline{y}_1$$

$$Y_2 = y_1 \oplus y_2$$


The resulting circuit is

 

8.21. From the state-assigned table given in the solution to Problem 8.20, the excitation table for JK flip-flops is

Present state $y_1y_0$	Flip-flop inputs		Output $z_1z_0$
	$J_1K_1$	$J_0K_0$	
0 0	1 $d$	0 $d$	0 0
1 0	$d$ 1	1 $d$	1 0
0 1	1 $d$	$d$ 0	0 1
1 1	$d$ 1	$d$ 1	1 1

 
The flip-flop inputs are  $J_1 = K_1 = 1$  and  $J_2 = K_2 = y_1$ . The resulting circuit is



8.22. From the state-assigned table given in the solution to Problem 8.20, the excitation table for T flip-flops is

Present state $y_1y_0$	Flip-flop inputs		Output $z_1z_0$
	$T_1$	$T_0$	
0 0	1	0	0 0
1 0	1	1	1 0
0 1	1	0	0 1
1 1	1	1	1 1

 The flip-flop inputs are  $T_1 = 1$  and  $T_2 = y_1$ . The resulting circuit is



8.23. The state diagram is

Present state	Next state		Output $z_2 z_1 z_0$
	$w = 0$	$w = 1$	
A	A	B	0 0 0
B	B	C	0 0 1
C	C	D	0 1 0
D	D	E	0 1 1
E	E	F	1 0 0
F	F	A	1 0 1

The state-assigned table is

Present state $y_2y_1y_0$	Next state		Output $z_2z_1z_0$
	$w = 0$	$w = 1$	
	$Y_2Y_1Y_0$		
000	000	001	000
001	001	010	001
010	010	011	010
011	011	100	011
100	100	101	100
101	101	000	101

The next-state expressions are

$$\begin{aligned}
 Y_2 &= \bar{y}_0 y_2 + \bar{w} y_2 + w y_0 y_1 \\
 Y_1 &= \bar{y}_0 y_1 + \bar{w} y_1 + w y_0 \bar{y}_1 \bar{y}_2 \\
 Y_0 &= \bar{w} y_0 + w \bar{y}_0
 \end{aligned}$$

The outputs are:  $z_2 = y_2$ ,  $z_1 = y_1$ , and  $z_0 = y_0$ .

8.24. Using the state-assigned table given in the solution for problem 8.23, the excitation table for JK flip-flops is

Present state $y_2y_1y_0$	Flip-flop inputs						Outputs $z_2z_1z_0$
	$w = 0$			$w = 1$			
	$J_2K_2$	$J_1K_1$	$J_0K_0$	$J_2K_2$	$J_1K_1$	$J_0K_0$	
000	0 $d$	0 $d$	0 $d$	0 $d$	0 $d$	1 $d$	000
001	0 $d$	0 $d$	$d$ 0	0 $d$	1 $d$	$d$ 1	001
010	0 $d$	$d$ 0	0 $d$	0 $d$	$d$ 0	1 $d$	010
011	0 $d$	$d$ 0	$d$ 0	1 $d$	$d$ 1	$d$ 1	011
100	$d$ 0	0 $d$	0 $d$	$d$ 0	0 $d$	1 $d$	100
101	$d$ 0	0 $d$	$d$ 0	$d$ 1	0 $d$	$d$ 1	101

The expressions for the inputs of the flip-flops are

$$J_2 = wy_1y_0$$

$$K_2 = wy_2y_0$$

$$J_1 = w\bar{y}_2y_0$$

$$K_1 = wy_0$$

$$J_0 = w$$

$$K_0 = w$$

The outputs are:  $z_2 = y_2$ ,  $z_1 = y_1$ , and  $z_0 = y_0$ .

8.25. Using the state-assigned table given in the solution for problem 8.23, the excitation table for T flip-flops is

Present state $y_2y_1y_0$	Flip-flop inputs		Outputs $z_2z_1z_0$
	$w = 0$	$w = 1$	
	$T_2T_1T_0$	$T_2T_1T_0$	
000	000	001	000
001	000	011	001
010	000	001	010
011	000	111	011
100	000	001	100
101	000	101	101

The expressions for  $T$  inputs of the flip-flops are

$$T_2 = wy_1y_0 + wy_2y_0$$

$$T_1 = w\bar{y}_2y_0$$

$$T_0 = w$$

The outputs are:  $z_2 = y_2$ ,  $z_1 = y_1$ , and  $z_0 = y_0$ .

8.26. The state diagram is

Present state	Next state		Count
	$w = 0$	$w = 1$	
A	H	C	0
B	A	D	1
C	B	E	2
D	C	F	3
E	D	G	4
F	E	H	5
G	F	A	6
H	G	B	7

The state-assigned table is

	Present state $y_2y_1y_0$	Next state		Output $z_2z_1z_0$
		$w = 0$	$w = 1$	
		$Y_2Y_1Y_0$	$Y_2Y_1Y_0$	
A	0 0 0	1 1 1	0 1 0	0 0 0
B	0 0 1	0 0 0	0 1 1	0 0 1
C	0 1 0	0 0 1	1 0 0	0 1 0
D	0 1 1	0 1 0	1 0 1	0 1 1
E	1 0 0	0 1 1	1 1 0	1 0 0
F	1 0 1	1 0 0	1 1 1	1 0 1
G	1 1 0	1 0 1	0 0 0	1 1 0
H	1 1 1	1 1 0	0 0 1	1 1 1

The next-state expressions (inputs to D flip-flops) are

$$D_2 = Y_2 = w\bar{y}_2y_1 + \bar{w}y_2y_1 + wy_2\bar{y}_1 + \bar{w}y_2y_0 + \bar{y}_2\bar{y}_1\bar{y}_0w$$

$$D_1 = Y_1 = w\bar{y}_1 + \bar{y}_1\bar{y}_0 + \bar{w}y_1y_0$$

$$D_0 = Y_0 = \bar{y}_0\bar{w} + y_0w$$

The outputs are:  $z_2 = y_2$ ,  $z_1 = y_1$ , and  $z_0 = y_0$ .



8.27. From the state-assigned table given in the solution to problem 8.26, the excitation table for JK flip-flops is

Present state $y_2y_1y_0$	Flip-flop inputs						Outputs $z_2z_1z_0$
	$w = 0$			$w = 1$			
	$J_2K_2$	$J_1K_1$	$J_0K_0$	$J_2K_2$	$J_1K_1$	$J_0K_0$	
000	1 $d$	1 $d$	1 $d$	0 $d$	1 $d$	0 $d$	000
001	0 $d$	0 $d$	$d$ 1	0 $d$	1 $d$	$d$ 0	001
010	0 $d$	$d$ 1	1 $d$	1 $d$	$d$ 1	0 $d$	010
011	0 $d$	$d$ 0	$d$ 1	1 $d$	$d$ 1	$d$ 0	011
100	$d$ 1	1 $d$	1 $d$	$d$ 0	1 $d$	0 $d$	100
101	$d$ 0	0 $d$	$d$ 1	$d$ 0	1 $d$	$d$ 0	101
110	$d$ 0	$d$ 1	1 $d$	$d$ 1	$d$ 1	0 $d$	110
111	$d$ 0	$d$ 0	$d$ 1	$d$ 1	$d$ 1	$d$ 0	111

The expressions for  $J$  and  $K$  inputs to the three flip-flops are

$$J_2 = y_1w + \overline{y_1}\overline{y_0}\overline{w}$$

$$K_2 = J_2$$

$$J_1 = w + \overline{y_0}$$

$$K_1 = J_1$$

$$J_0 = \overline{w}$$

$$K_0 = J_0$$

The outputs are:  $z_2 = y_2$ ,  $z_1 = y_1$ , and  $z_0 = y_0$ .

8.28. From the state-assigned table given in the solution to problem 8.26, the excitation table for T flip-flops is

Present state $y_2y_1y_0$	Flip-flop inputs		Outputs $z_2z_1z_0$
	$w = 0$	$w = 1$	
	$T_2T_1T_0$	$T_2T_1T_0$	
000	111	010	000
001	001	010	001
010	011	110	010
011	001	110	011
100	111	010	100
101	001	010	101
110	011	110	110
111	001	110	111

The expressions for  $T$  inputs of the flip-flops are

$$T_2 = \overline{y_1}\overline{y_0}\overline{w} + y_1w$$

$$T_1 = w + \overline{y_0}$$

$$T_0 = \overline{w}$$

The outputs are:  $z_2 = y_2$ ,  $z_1 = y_1$ , and  $z_0 = y_0$ .

8.29. The next-state and output expressions are

$$\begin{aligned} D_1 &= Y_1 = w(y_1 + y_2) \\ D_2 &= Y_2 = w(\overline{y}_1 + \overline{y}_2) \\ z &= y_1 \overline{y}_2 \end{aligned}$$

The corresponding state-assigned table is

Present state $y_2 y_1$	Next state		Output $z$
	$w = 0$	$w = 1$	
	$Y_2 Y_1$	$Y_2 Y_1$	
0 0	0 0	1 0	0
0 1	0 0	1 1	1
1 0	0 0	1 1	0
1 1	0 0	0 1	0

This leads to the state table

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	C	0
B	A	D	1
C	A	D	0
D	A	B	0

The circuit produces  $z = 1$  whenever the input sequence on  $w$  comprises a 0 followed by an even number of 1s.

8.30. The Verilog code based on the style of code in Figure 8.29 is

```
module prob8_30 (Clock, Resetn, D, N, z);
  input Clock, Resetn, D, N;
  output z;
  reg [3:1] y, Y;
  wire [1:0] K;
  parameter [3:1] S1 = 3'b000, S2 = 3'b001, S3 = 3'b010, S4 = 3'b011, S5 = 3'b100;

  // Define the next state combinational circuit
  assign K = {D, N};
  always @(K or y)
    case (y)
      S1: if (K == 2'b00) Y = S1;
          else if (K == 2'b01) Y = S3;
          else if (K == 2'b10) Y = S2;
          else Y = 3'bxxx;
      S2: if (K == 2'b00) Y = S2;
          else if (K == 2'b01) Y = S4;
          else if (K == 2'b10) Y = S5;
          else Y = 3'bxxx;
      S3: if (K == 2'b00) Y = S3;
          else if (K == 2'b01) Y = S2;
          else if (K == 2'b10) Y = S4;
          else Y = 3'bxxx;
      S4: if (K == 2'b00) Y = S1;
          else Y = 3'bxxx;
      S5: if (K == 2'b00) Y = S3;
          else Y = 3'bxxx;
      default: Y = 3'bxxx;
    endcase

  // Define the sequential block
  always @(negedge Resetn or posedge Clock)
    if (Resetn == 0) y <= S1;
    else y <= Y;

  // Define output
  assign z = (y == S4) | (y == S5);

endmodule
```

8.31. The Verilog code based on the style of code in Figure 8.34 is

```

module prob8_31 (Clock, Resetn, D, N, z);
  input Clock, Resetn, D, N;
  output z;
  reg [3:1] y;
  wire [1:0] K;
  parameter [3:1] S1 = 3'b000, S2 = 3'b001, S3 = 3'b010, S4 = 3'b011, S5 = 3'b100;

  assign K = {D, N};
  // Define the sequential block
  always @(negedge Resetn or posedge Clock)
    if (Resetn == 0) y <= S1;
    else
      case (y)
        S1: if (K == 2'b00) y <= S1;
            else if (K == 2'b01) y <= S3;
            else if (K == 2'b10) y <= S2;
            else y <= 3'bxxx;
        S2: if (K == 2'b00) y <= S2;
            else if (K == 2'b01) y <= S4;
            else if (K == 2'b10) y <= S5;
            else y <= 3'bxxx;
        S3: if (K == 2'b00) y <= S3;
            else if (K == 2'b01) y <= S2;
            else if (K == 2'b10) y <= S4;
            else y <= 3'bxxx;
        S4: if (K == 2'b00) y <= S1;
            else y <= 3'bxxx;
        S5: if (K == 2'b00) y <= S3;
            else y <= 3'bxxx;
        default: y <= 3'bxxx;
      endcase

  // Define output
  assign z = (y == S4) | (y == S5);

endmodule

```

8.32. The Verilog code based on the style of code in Figure 8.29 is

```

module prob8_32 (Clock, Resetn, D, N, z);
  input Clock, Resetn, D, N;
  output z;
  reg z;
  reg [2:1] y, Y;
  wire [1:0] K;
  parameter [2:1] S1 = 2'b00, S2 = 2'b01, S3 = 2'b10;

  cont'd

```

```

// Define the next state and output combinational circuits
assign K = {D, N};
always @(K or y)
  case (y)
    S1: if (K == 2'b00)      begin
      Y = S1;  z = 0;
    end
    else if (K == 2'b01)    begin
      Y = S3;  z = 0;
    end
    else if (K == 2'b10)    begin
      Y = S2;  z = 0;
    end
    else                   begin
      Y = 2'bxx;  z = 1'bx;
    end
    S2: if (K == 2'b00)    begin
      Y = S2;  z = 0;
    end
    else if (K == 2'b01)    begin
      Y = S1;  z = 1;
    end
    else if (K == 2'b10)    begin
      Y = S3;  z = 1;
    end
    else                   begin
      Y = 2'bxx;  z = 1'bx;
    end
    S3: if (K == 2'b00)    begin
      Y = S3;  z = 0;
    end
    else if (K == 2'b01)    begin
      Y = S2;  z = 0;
    end
    else if (K == 2'b10)    begin
      Y = S1;  z = 1;
    end
    else                   begin
      Y = 2'bxx;  z = 1'bx;
    end
    default:              begin
      Y = 2'bxx;  z = 1'bx;
    end
  endcase

// Define the sequential block
always @(negedge Resetn or posedge Clock)
  if (Resetn == 0)  y <= S1;
  else  y <= Y;
endmodule

```

8.33. The Verilog code based on the style of code in Figure 8.34 is

```
module prob8_33 (Clock, Resetn, D, N, z);
  input Clock, Resetn, D, N;
  output z;
  reg [2:1] y;
  wire [1:0] K;
  parameter [2:1] S1 = 2'b00, S2 = 2'b01, S3 = 2'b10;

  assign K = {D, N};
  // Define the sequential block
  always @(negedge Resetn or posedge Clock)
    if (Resetn == 0) y <= S1;
    else
      case (y)
        S1: if (K == 2'b00) y <= S1;
           else if (K == 2'b01) y <= S3;
           else if (K == 2'b10) y <= S2;
           else y <= 2'bxx;
        S2: if (K == 2'b00) y <= S2;
           else if (K == 2'b01) y <= S1;
           else if (K == 2'b10) y <= S3;
           else y <= 2'bxx;
        S3: if (K == 2'b00) y <= S3;
           else if (K == 2'b01) y <= S2;
           else if (K == 2'b10) y <= S1;
           else y <= 2'bxx;
        default: y <= 2'bxx;
      endcase


  // Define output
  assign z = ((y == S2) & ((K == 2'b01) | (K == 2'b10))) | ((y == S3) & (K == 2'b10));

endmodule
```

8.34. Verilog code for the FSM in Figure P8.2 is


```
module prob8_34 (Clock, Resetn, w, z);  
  input Clock, Resetn, w;  
  output z;  
  reg [2:1] y, Y;  
  parameter [2:1] A = 2'b00, B = 2'b01, C = 2'b10, D = 2'b11;  
  
  // Define the next state combinational circuit  
  always @(w or y)  
    case (y)  
      A: if (w) Y = C;  
         else Y = A;  
      B: if (w) Y = D;  
         else Y = A;  
      C: if (w) Y = D;  
         else Y = A;  
      D: if (w) Y = B;  
         else Y = A;  
    endcase  
  
  // Define the sequential block  
  always @(negedge Resetn or posedge Clock)  
    if (Resetn == 0) y <= A;  
    else y <= Y;  
  
  // Define output  
  assign z = (y == B);  
endmodule
```

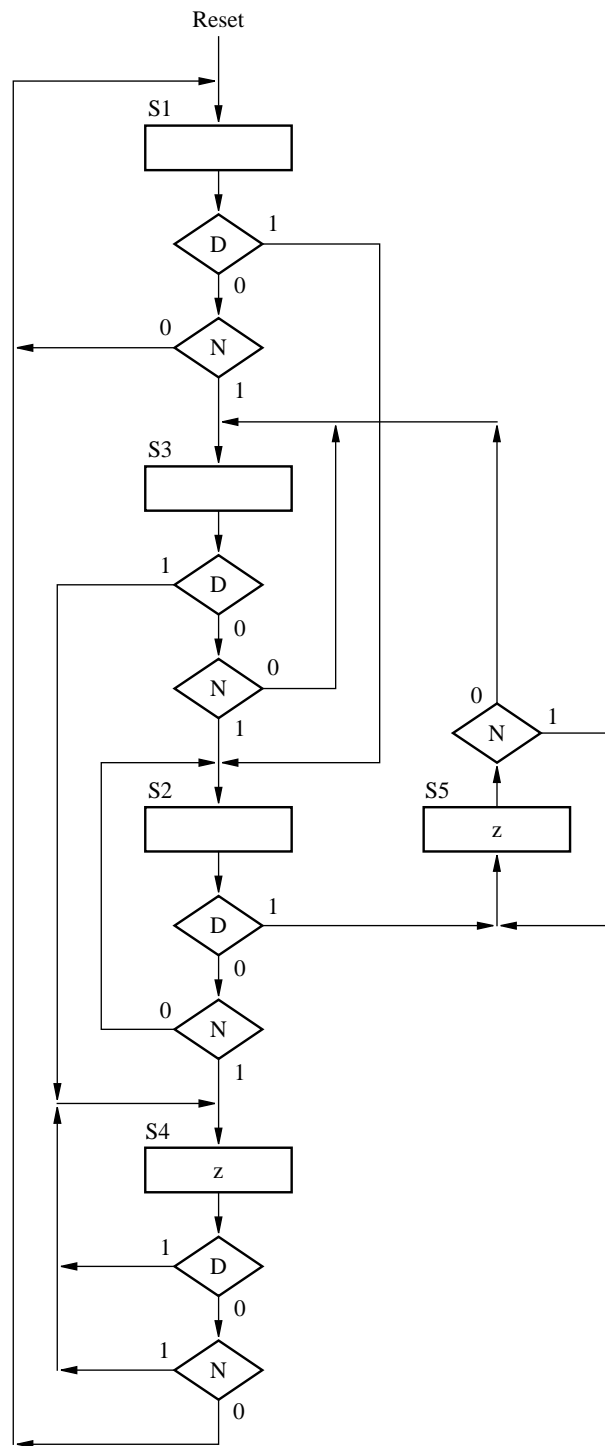8.35. An ASM chart for the FSM in Figure 8.57 is






 
8.36. An ASM chart for the FSM in Figure 8.58 is



 8.37. To ensure that the device 3 will get serviced the FSM in Figure 8.72 can be modified as follows:



 8.39. The required control signals can be generated using the following FSM:



Let  $k = w_2 + w_1$ . Then the next-state transitions can be defined as

Present state	Next state	
	$k = 0$	$k = 1$
A	A	B
B	B	C
C	C	A

Using one-hot encoding, the state-assigned table becomes

Present state $y_3y_2y_1$	Next state	
	$k = 0$	$k = 1$
	$Y_3Y_2Y_1$	$Y_3Y_2Y_1$
001	001	010
010	010	100
100	100	001

The next-state expressions are

$$\begin{aligned} Y_3 &= \bar{k}y_3 + ky_2 \\ Y_2 &= \bar{k}y_2 + ky_1 \\ Y_1 &= \bar{k}y_1 + ky_3 \end{aligned}$$

The output expressions are

$$\begin{aligned} TEMP_{in} &= ky_1 \\ TEMP_{out} &= ky_3 \\ R1_{out} &= y_2(w_2 \oplus w_1) \\ R1_{in} &= y_3(w_2 \oplus w_1) \\ R2_{out} &= y_1\bar{w}_2w_1 + y_2w_2w_1 \\ R2_{in} &= y_2\bar{w}_2w_1 + y_3w_2w_1 \\ R3_{out} &= y_1w_2 \\ R3_{in} &= y_2w_2 \end{aligned}$$