 



# Chapter 7

7.1.




7.2. The circuit in Figure 7.3 can be modified to implement an SR latch by connecting  $S$  to the *Data* input and  $S + R$  to the *Load* input. Thus the value of  $S$  is loaded into the latch whenever either  $S$  or  $R$  is asserted. Care must be taken to ensure that the *Data* signal remains stable while the *Load* signal is asserted.


7.3.

 


7.4.

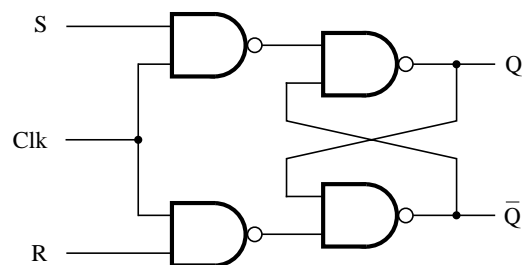


7.5.

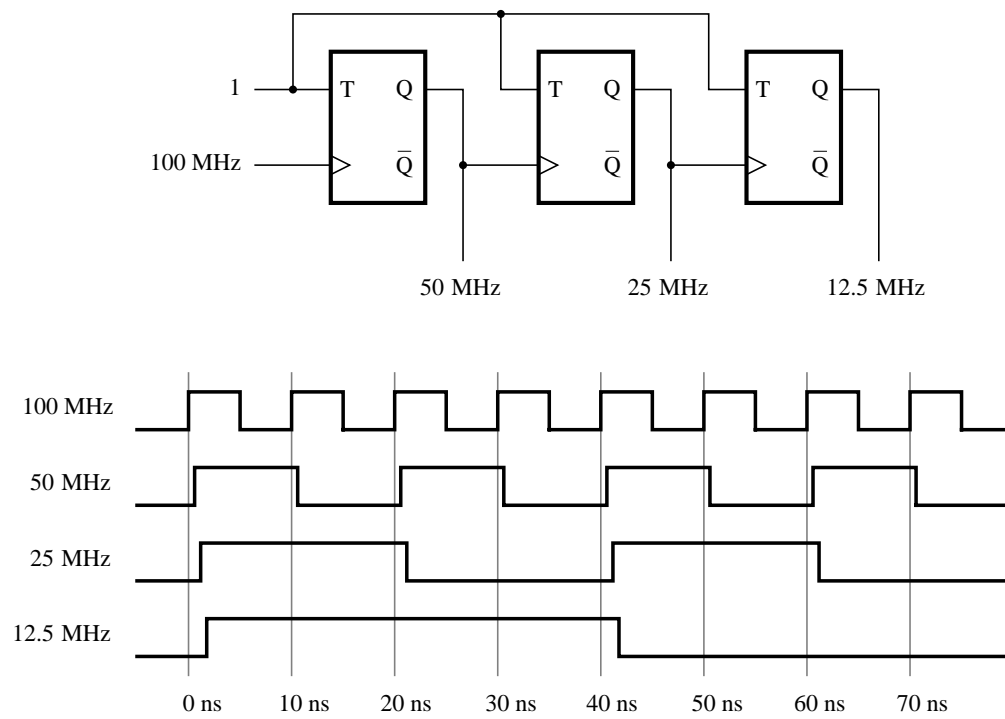


7.6.

 


S	R	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	0

 

7.7.

 

7.8.

 

7.9. This circuit acts as a negative-edge-triggered JK flip-flop, in which  $J = A$ ,  $K = B$ ,  $Clock = C$ ,  $Q = D$ , and  $\bar{Q} = E$ . This circuit is found in the standard chip called 74LS107A (plus a *Clear* input, which is not shown).

7.10.

```
module tflipflop (T, Clock, Resetn, Q);
  input T, Clock, Resetn;
  output Q;
  reg Q;

  always @(negedge Resetn or posedge Clock)
    if (!Resetn)
      Q <= 0;
    else if (T)
      Q <= Q;

endmodule
```

7.11.

```
module jkflipflop (J, K, Clock, Resetn, Q);
  input J, K, Clock, Resetn;
  output Q;
  reg Q;

  always @(negedge Resetn or posedge Clock)
    if (!Resetn)
      Q <= 0;
    else
      case (J, K)
        1'b01:   Q <= 0;
        1'b10:   Q <= 1;
        1'b11:   Q <= Q;
        default: Q <= Q;
      endcase

endmodule
```

7.13. Let  $S = s_1s_0$  be a binary number that specifies the number of bit-positions by which to rotate. Also let  $L$  be a parallel-load input, and let  $R = r_0r_1r_2r_3$  be parallel data. If the inputs to the flip-flops are  $d_0 \dots d_3$  and the outputs are  $q_0 \dots q_3$ , then the barrel-shifter can be represented by the logic expressions

$$\begin{aligned} d_0 &= L \cdot r_0 + \overline{L} \cdot (\overline{s_1}\overline{s_0}q_0 + \overline{s_1}s_0q_3 + s_1\overline{s_0}q_2 + s_1s_0q_1) \\ d_1 &= L \cdot r_1 + \overline{L} \cdot (\overline{s_1}\overline{s_0}q_1 + \overline{s_1}s_0q_0 + s_1\overline{s_0}q_3 + s_1s_0q_2) \\ d_2 &= L \cdot r_2 + \overline{L} \cdot (\overline{s_1}\overline{s_0}q_2 + \overline{s_1}s_0q_1 + s_1\overline{s_0}q_0 + s_1s_0q_3) \\ d_3 &= L \cdot r_3 + \overline{L} \cdot (\overline{s_1}\overline{s_0}q_3 + \overline{s_1}s_0q_2 + s_1\overline{s_0}q_1 + s_1s_0q_0) \end{aligned}$$

7.14. There are many ways to write the Verilog code for this problem. One solution is

```

// Barrel shifter. If L = 1, load in parallel from R. If L = 0 and E = 1
// rotate right by number of bit positions given by S.
module barrel4 (R, L, S, Clock, Q);
    input [0:3] R;
    input L, Clock;
    input [1:0] S;
    output [0:3] Q;
    reg [0:3] Q;
    wire [0:3] M;

    mux4to1 Bit0 (Q[0], Q[3], Q[2], Q[1], S, M[0]);
    mux4to1 Bit1 (Q[1], Q[0], Q[3], Q[2], S, M[1]);
    mux4to1 Bit2 (Q[2], Q[1], Q[0], Q[3], S, M[2]);
    mux4to1 Bit3 (Q[3], Q[2], Q[1], Q[0], S, M[3]);

    always @(posedge Clock)
        if (L)
            Q <= R;
        else
            begin
                Q[0] <= M[0];
                Q[1] <= M[1];
                Q[2] <= M[2];
                Q[3] <= M[3];
            end

endmodule


module mux4to1 (w0, w1, w2, w3, S, f);
    input w0, w1, w2, w3;
    input [1:0] S;
    output f;
    reg f;

    always @(w0 or w1 or w2 or w3 or S)
        if (S == 2'b00)
            f = w0;
        else if (S == 2'b01)
            f = w1;
        else if (S == 2'b10)
            f = w2;
        else if (S == 2'b11)
            f = w3;


endmodule

```


7.15.

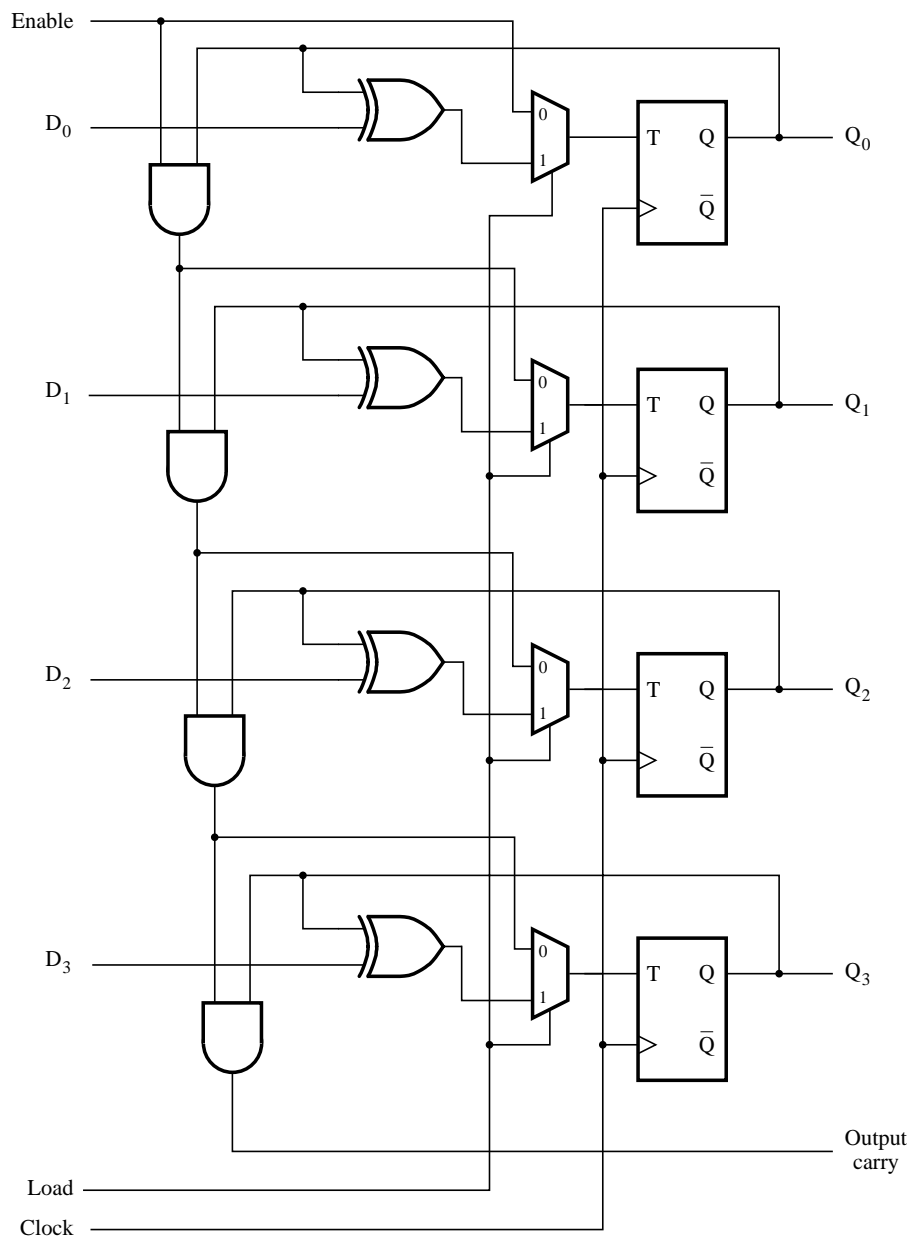

7.16.

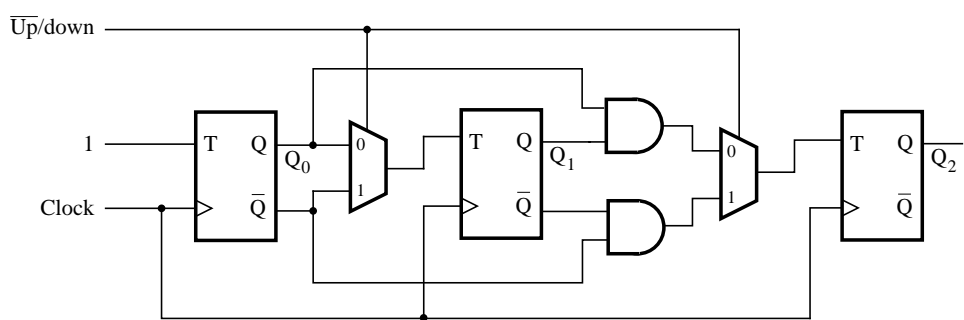


7.17.

 

7.18. The counting sequence is 000, 001, 010, 111.

7.19. The circuit in Figure P7.4 is a master-slave JK flip-flop. It suffers from a problem sometimes called *ones-catching*. Consider the situation where the Q output is low,  $Clock = 0$ , and  $J = K = 0$ . Now let  $Clock$  remain stable at 0 while  $J$  change from 0 to 1 and then back to 0. The master stage is now set to 1 and this value will be incorrectly transferred into the slave stage when the clock changes to 1.

 7.20. Repeated application of DeMorgan's theorem can be used to change the positive-edge triggered D flip-flop in Figure 7.11 into the negative-edge D triggered flip-flop:



7.21.

```
module upcount12 (Resetn, Clock, Q);
  input Resetn, Clock;
  output [3:0] Q;
  reg [3:0] Q;

  always @(posedge Clock)
    if (!Resetn)
      Q <= 0;
    else if (Q == 11)
      Q <= 0;
    else
      Q <= Q + 1;
endmodule
```

7.22. The longest delay in the circuit is the from the output of FF<sub>0</sub> to the input of FF<sub>3</sub>. This delay totals 5 ns. Thus the minimum period for which the circuit will operate reliably is

$$T_{min} = 5 \text{ ns} + t_{su} = 8 \text{ ns}$$

The maximum frequency is

$$F_{max} = 1/T_{min} = 125 \text{ MHz}$$

7.23.

```
module johnson8 (Resetn, Clock, Q);
  input Resetn, Clock;
  output [7:0] Q;
  reg [7:0] Q;

  always @(negedge Resetn or posedge Clock)
    if (!Resetn)
      Q <= 0;
    else
      Q <= {{Q[6:0]}, {~Q[7]}};
endmodule
```



7.24.

```
// Ring counter with synchronous reset
module ripplen (Resetn, Clock, Q);
  parameter n = 8;
  input Resetn, Clock;
  output [n-1:0] Q;
  reg [n-1:0] Q;

  always @(posedge Clock)
    if (!Resetn)
      begin
        Q[7:1] <= 0;
        Q[0] <= 1;
      end
    else
      Q <= {{Q[6:0]}, {Q[7]}};
endmodule
```

7.25.

```
module accumulate(Reset, Clock, Data, Q);
  input Reset, Clock;
  input [3:0] Data;
  output [3:0] Q;
  reg [3:0] Q;

  always @(posedge Reset or posedge Clock)
    if (Reset)
      Q <= 0;
    else
      Q <= Q + Data;
endmodule
```

7.26.

```
module count32 (Clock, Reset, Q);
  input Clock, Reset;
  output [31:0] Q ;

  lpm_counter count_up (.aclr(Reset), .clock(Clock), .q(Q)) ;
  defparam count_up.lpm_width = 32;
endmodule
```

7.30.

	$T_1$	$T_2$	$T_3$
(Swap): $I_4$	$R_{out} = X, T_{in}$	$R_{out} = Y, R_{in} = X$	$T_{out}, R_{in} = Y,$ $Done$

Since the processor now has five operations a 3-to-8 decoder is needed to decode the signals  $f_2, f_1, f_0$ . The SWAP operation is represented by the code

$$I_4 = f_2 \bar{f}_1 \bar{f}_0$$

New expressions are needed for  $R_{in}$  and  $R_{out}$  to accommodate the SWAP operation:


$$\begin{aligned} Rk_{in} &= (I_0 + I_1) \cdot T_1 \cdot X_k + (I_2 + I_3) \cdot T_3 \cdot X_k + I_4 \cdot T_2 \cdot X_k + I_4 \cdot T_3 \cdot Y_k \\ Rk_{out} &= I_1 \cdot T_1 \cdot Y_k + (I_2 + I_3) \cdot (T_1 X_k + T_2 Y_k) + I_4 \cdot T_1 X_k + I_4 \cdot T_2 Y_k \end{aligned}$$

The control signals for the temporary register,  $T$ , are

$$\begin{aligned} T_{in} &= T_1 I_4 \\ T_{out} &= T_3 I_4 \end{aligned}$$

7.31. (a) Period =  $2 \times n \times t_p$



(b)

 


The counter tallies the number of pulses in the 100 ns time period. Thus

$$t_p = \frac{100 \text{ ns}}{2 \times \text{Count} \times n}$$

7.32.

  


7.33.

 


7.34. With non-blocking assignments, the result of the assignment  $f \leq A[1] \& A[0]$  is not seen by the successive assignments inside the **for** loop. Thus,  $f$  has an uninitialized value when the **for** loop is entered. Similarly, each **for** loop iteration sees the uninitialized value of  $f$ . The result of the code is the sequential circuit specified by  $f = f \mid A[n-1] A[n-2]$ .

7.35.

 


The counting sequence is: 001, 110, 011, 111, 101, 100, 010, 001

7.36.

 


The counting sequence is: 001, 101, 111, 110, 011, 100, 010, 001

7.37.

 


The counting sequence is: 001, 100, 000, 000, ...

7.38.

 

The counting sequence is: 001, 110, 000, 000, ...

7.39.

 

7.40.

```

// Universal shift register. If Dir = 0 shifting is to the left.
module universaln (R, L, Dir, w0, w1, Clock, Q);
    parameter n = 4;
    input [n-1:0] R;
    input L, Dir, w0, w1, Clock;
    output [n-1:0] Q;
    reg [n-1:0] Q;
    integer k;

    always @(posedge Clock)
        if (L)
            Q <= R;
        else
            begin
                if (Dir)
                    begin
                        for (k = 0; k < n-1; k = k+1)
                            Q[k] <= Q[k+1];
                        Q[n-1] <= w0;
                    end
                else
                    begin
                        Q[0] <= w1;
                        for (k = n-1; k > 0; k = k-1)
                            Q[k] <= Q[k-1];
                    end
            end
        end
endmodule

```