 


Chapter 11

11.1. Label the wires in the circuit of Figure P11.1 as follows:




A complete fault table is

Test $w_1w_2w_3$	Fault detected									
	$a/0$	$a/1$	$b/0$	$b/1$	$c/0$	$c/1$	$d/0$	$d/1$	$f/0$	$f/1$
000								✓	✓	
001					✓		✓			✓
010								✓	✓	
011		✓			✓		✓			✓
100								✓	✓	
101				✓	✓		✓			✓
110									✓	
111	✓		✓			✓			✓	

A minimal test set must include the tests $w_1w_2w_3 = 011, 101$, and 111 , which cover all faults except $d/1$. The latter fault can be detected by choosing one of $000, 010$, or 100 .

 11.2. Label the wires in the circuit of Figure P11.2 as follows:




A complete fault table is

Test $w_1w_2w_3w_4$	Fault detected													
	$a/0$	$a/1$	$b/0$	$b/1$	$c/0$	$c/1$	$d/0$	$d/1$	$e/0$	$e/1$	$g/0$	$g/1$	$f/0$	$f/1$
0000														✓
0001		✓		✓					✓					✓
0010		✓		✓					✓					✓
0011		✓		✓					✓					✓
0100						✓		✓			✓			✓
0101			✓				✓			✓		✓	✓	
0110			✓		✓					✓		✓	✓	
0111			✓							✓			✓	
1000						✓		✓			✓			✓
1001	✓						✓			✓		✓	✓	
1010	✓				✓					✓		✓	✓	
1011	✓									✓			✓	
1100						✓		✓			✓			✓
1101							✓					✓	✓	
1110					✓							✓	✓	
1111										✓		✓	✓	

A possible minimal test set consists of $w_1w_2w_3w_4 = 0001, 0110, 1000$, and 1001 .

11.3. The two functions differ only in the vertex $x_1x_2x_3x_4 = 0111$. Therefore, the circuits can be distinguished by applying this input valuation.

 11.4. Label the wires in the circuit of Figure P11.3 as follows:



Path $w_1 - a - d - f$ is sensitized with $w_2w_3w_4w_5 = 111x$
 Path $w_2 - a - d - f$ is sensitized with $w_1w_3w_4w_5 = 111x$
 Path $w_3 - b - c - d - f$ is sensitized with $w_1w_2w_4w_5 = 0x11$
 Path $w_3 - b - e - f$ is sensitized with $w_1w_2w_4w_5 = 1110$
 Path $w_4 - b - c - d - f$ is sensitized with $w_1w_2w_3w_5 = 0x11$
 Path $w_4 - b - e - f$ is sensitized with $w_1w_2w_3w_5 = 1110$
 Path $w_5 - e - f$ is sensitized with $w_1w_2w_3w_4 = xx0x$

As an input signal to each path it is necessary to apply both 0 and 1 to give two tests. A possible test set is $w_1w_2w_3w_4w_5 = 01111, 11110, 1011x, 0x011, 11010, 0x101, \text{ and } 11100$

11.5. The tests are $w_1w_2w_3w_4 = 1111, 1110, 0111, \text{ and } 1111$.

11.6. Test 0100 detects $w_1/1, c/1, d/1, w_4/1, \text{ and } f/1$.

Test 1010 detects $b/0, d/0, w_3/0, \text{ and } f/0$.

Test 0011 detects $f/0$.

Test 1111 detects $f/0$.

Test 0110 detects $w_1/1, w_2/0, b/1, c/1, d/1, w_4/1, \text{ and } f/1$.

Thus 11 different single faults can be detected using these four tests. Since the circuit has 8 wires, there can be 16 single $s/0$ or $s/1$ faults. Therefore, the tests cover 69% of single faults.

11.7. Test 0100 detects $w_1/1, b/0, c/0, g/1, h/0, k/0, \text{ and } f/1$.


Test 1010 detects $w_2/1, w_4/1, b/0, c/0, g/1, h/0, k/0, \text{ and } f/1$.

Test 0011 detects $w_3/0, w_4/0, b/0, c/1, g/0, h/1, \text{ and } f/0$.

Test 0110 detects $w_1/1, w_4/1, b/0, c/0, g/1, h/0, k/0, \text{ and } f/1$.

Thus 15 different single faults can be detected using these four tests. Since the circuit has 10 wires, there can be 20 single $s/0$ or $s/1$ faults. Therefore, the tests cover 75% of single faults.

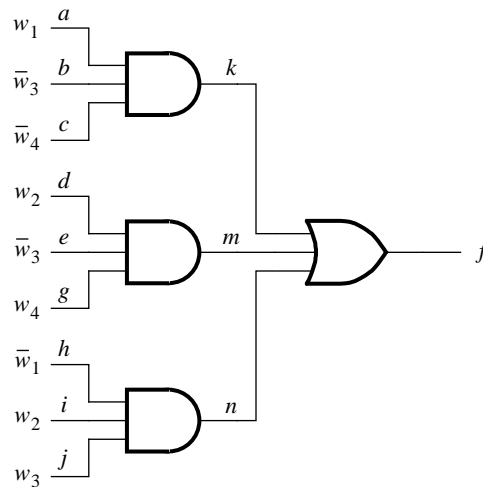11.8. Label the wires in the circuit of Figure 11.5 as follows:



Test 0100 detects $a/1, g/1, j/1, k/1, m/1, n/1$, and $f/1$.

Test 1010 detects $b/1, k/1, m/1, n/1$, and $f/1$.

Test 0011 detects $i/1, k/1, m/1, n/1$, and $f/1$.

Test 0110 detects $h/0, i/0, j/0, n/0$, and $f/0$.

Thus 14 different single faults can be detected using these four tests. Since the circuit has 13 wires, there can be 26 single $s/0$ or $s/1$ faults. Therefore, the tests cover 54% of single faults.

11.9. Cannot detect if the input wire w_1 is stuck-at-1. The reason is that this circuit is highly redundant. It realizes the function $f = w_3(\overline{w}_1 + \overline{w}_2)$, which can be implemented with a simpler circuit.

11.10. In a circuit in which all gates have a fan-out of 1 there exists a single path from any primary input to the output of the circuit. A test for a fault on a primary input sensitizes the path that leads from this input to the output of the circuit, thus testing for faults along this path. Therefore, a test set that tests all faults on the primary inputs, will also test all faults on the sensitized paths.

11.11. Test set = {0000, 0111, 1111, 1000}. It would work with XORs implemented as shown in Figure 4.28c.

For n bits, the same patterns can be used; thus

Test set = {00...00, 011...1, 11...11, 100...0}.

11.12. In the decoder circuit in Figure 6.16c the four AND gates are enabled only if the En signal is active. The required test set has to include all four valuations of w_1 and w_2 when $En = 1$. It is also necessary to test if the En wire is stuck at 1, which can be accomplished with the test $w_1w_2En = 000$. Therefore, a complete test set comprises $w_1w_2En = 000, 001, 011, 101$, and 111 .

11.13. Test 1100 detects $w_1/0, w_2/0, b/1, c/0, g/0, k/1$, and $f/0$.

Test 0010 detects $w_4/1, b/0, c/0, g/1, h/0, k/0$, and $f/1$.

Test 0110 detects $w_1/1, w_4/1, b/0, c/0, g/1, h/0, k/0$, and $f/1$.

11.14. Label the output wires of the top three AND gates in Figure 11.12 as a, b , and c , respectively. Then the paths in the combinational part of the circuit are sensitized as follows.

Path $\overline{y}_1 - a - Y_1$ is sensitized with $w = 1$ and $y_2 = 0$.

Path $w - a - Y_1$ is sensitized with $y_1 = 0$ and $y_2 = 0$.

Path $w - b - Y_1$ is sensitized with $y_1 = 1$ and $y_2 = 1$.

Path $w - b - Y_2$ is sensitized with $y_1 = 0$ and $y_2 = 1$.

Path $y_2 - b - Y_1$ is sensitized with $w = 1$ and $y_1 = 1$.

Path $y_2 - b - Y_2$ is sensitized with $w = 1$ and $y_1 = 0$.

Path $w - c - Y_2$ is sensitized with $y_1 = 1$ and $y_2 = 0$.


Path $y_1 - c - Y_2$ is sensitized with $w = 1$ and $y_2 = 0$.

Path $y_1 = z$ is sensitized with $y_2 = 1$.

Path $y_2 = z$ is sensitized with $y_1 = 1$.

All 8 valuations of signals w, y_1 and y_2 have to be applied to sensitize these paths. It takes 26 clock cycles to perform the tests.

 - 11.15. For simplicity, in the ASM chart it is assumed that testing begins one clock cycle after *Resetn* is de-asserted. States S2 to S6 depict the actions listed on page 666. We assume that external circuitry places the test data values on the *Scan-in* and *w* ports, and checks the generated results at *Scan-out* and *z*.



Notes

Note 1: Scan-in has test value for y_2

Note 2: Scan-in has test value for y_1

Note 3: w has test value

Note 4: Scan-out has test result for y_2

Note 5: Scan-out has test result for y_1

11.16. Assume that the circuit has been reset by applying $Resetn = 0$. Then, let $Resetn = 1$ and observe the behavior indicated in the following table.

Clock cycle	$\overline{\text{Normal}}/\text{Scan}$	Scan-in	Scan-out	w	z	Transition tested
1	1	0	0	x	x	Reset
2	1	0	0	x	x	
3	0	x	x	0	0	$A \rightarrow A$
4	1	0	0	x	x	
5	1	1	0	x	x	
6	0	x	x	0	0	$B \rightarrow A$
7	1	0	0	x	x	
8	1	0	0	x	x	
9	0	x	x	1	0	$A \rightarrow B$
10	1	0	0	x	x	
11	1	1	1	x	x	
12	0	x	x	1	0	$B \rightarrow C$
13	1	1	1	x	x	
14	1	0	0	x	x	
15	0	x	x	0	0	$C \rightarrow A$
16	1	1	0	x	x	
17	1	0	0	x	x	
18	0	x	x	1	0	$C \rightarrow D$
19	1	1	1	x	x	
20	1	1	1	x	x	
21	0	x	x	0	1	$D \rightarrow A$
22	1	1	0	x	x	
23	1	1	0	x	x	
24	0	x	x	1	1	$D \rightarrow D$
25	1	x	1	x	x	
26	1	x	1	x	x	

11.17. The Verilog code for Figure 11.12 is

```

module prob11_17 (w, scanin, norm_scan, z, scanout, Resetn, Clock);
  input w, scanin, norm_scan, Resetn, Clock;
  output z, scanout;
  reg z, scanout;
  reg [2:1] y, Y, D;


  // Define the combinational circuitry
  always @(w or y or scanin or norm_scan)
  begin
    Y[1] = (w & ~y[1]) | (w & y[2]);
    Y[2] = (w & y[2]) | (w & y[1]);
    z = y[1] & y[2];
    if (norm_scan == 0)
    begin
      D[1] = Y[1];
      D[2] = Y[2];
    end
    else
    begin
      D[1] = scanin;
      D[2] = y[1];
    end
    scanout = y[2];
  end

  // Define the flip-flops
  always @(negedge Resetn or posedge Clock)
    if (Resetn == 0) y <= 0;
    else y <= D;

endmodule

```

 11.18. For simplicity, it is assumed in the ASM chart that testing begins when the reset signal is de-asserted. The ASM chart corresponds to the first three steps listed on page 675; the other steps are similar and are not shown. In the ASM chart, B1M represents the two-bit signal M_1M_2 for BILBO1 and B2M represents M_1M_2 for BILBO2. Similarly, $\overline{G}/S1$ and $\overline{G}/S2$ represent the \overline{G}/S signals for BILBO1 and BILBO2. Assume that there are n flip-flops in each BILBO register and that k clock cycles are used when running each BILBO circuit as a PRBS generator.



Notes

- Note 1: Initial test data for CN1 placed on *Scan-in* over n clock cycles
- Note 2: Initial test data for CN2 placed on *Scan-in* over n clock cycles. Observe generated results for CN1 on *Scan-out*
- Note 3: BILBO1 is shifted into BILBO2 for n clock cycles and 0 is placed on *Scan-in*